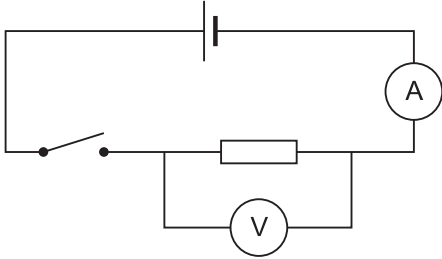

Comparing different energy resources

Advantages and disadvantages of different sources of energy

- How cheap is the energy source?
- How polluting is it? Consider the environmental consequences of both the extraction and the use of the energy.
- How sustainable is it? Will it run out soon or is it renewable?
- How convenient is it? We often need energy in large quantities but many non-polluting forms of energy are only available in small quantities (e.g. solar cells, wind, waves).
- Is it easy to turn into a useful form, such as electricity or fuel for a vehicle?

Ohm's law

1 Set up a circuit as shown in the diagram below using the resistance wire given to you as the resistor.





- 2 Measure the current in the circuit.
- 3 Measure the potential difference (voltage) across the conductor.
- 4 Record your results in a table like the one below.

No. of cells	Voltage (V)	Current (I)	Voltage/current (V/I)
1			
2			
3			
4			
5			

- 5 Repeat steps 1–4 with two cells, three cells, four cells and five cells.
- 6 Divide voltage by current in each case and write the results in the appropriate row in the last column.
- 7 Plot a line graph of the voltage (*y*-axis) against the current (*x*-axis). What conclusions can be drawn from the graph?

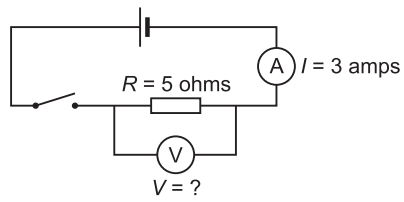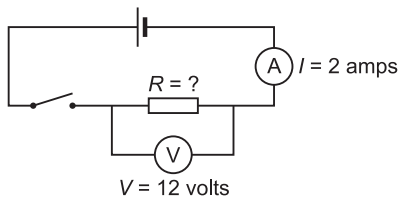Questions

- 1 In the following circuits, find the missing values of R and V .



- 2 In the same circuit, if $R = 4 \text{ ohms}$ and the voltage across the wire is 12 volts, what is the current I through the circuit.
- 3 In the same circuit, if $R = 10 \text{ ohms}$ and the voltage across the wire is 5 volts, what is the current I through the circuit.

